
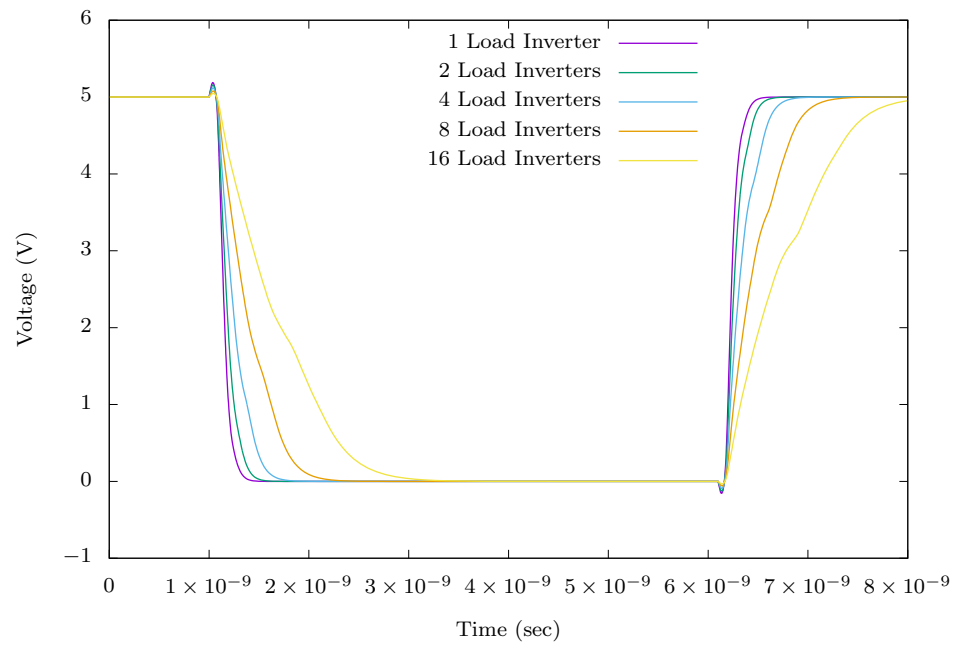


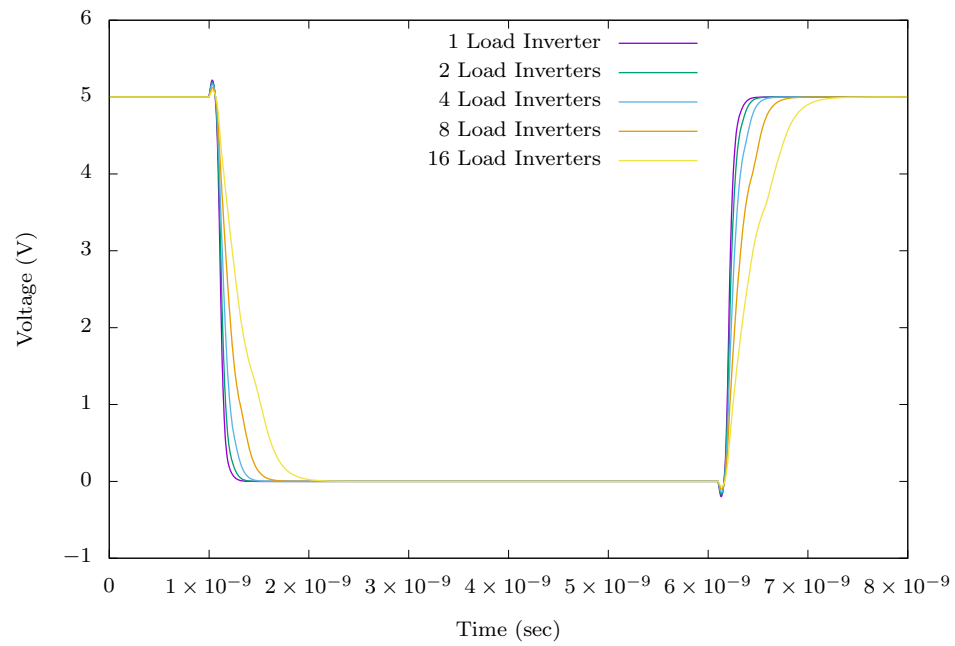
Output Voltage vs. Time of Inverter x1 with Differing Loads and Square Wave Input




Output Voltage vs. Time of Inverter x2 with Differing Loads and Square Wave Input



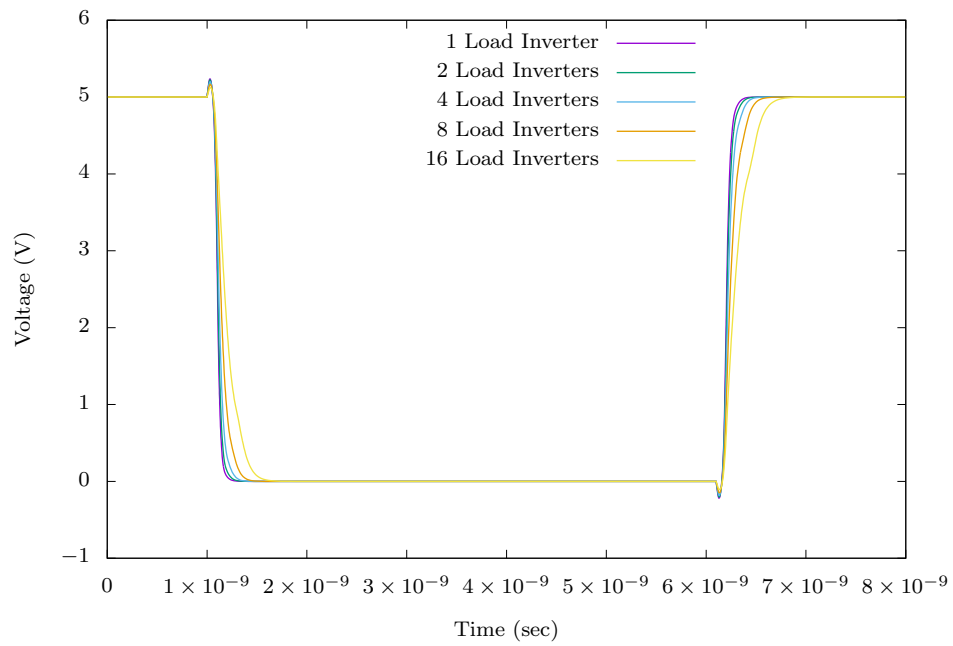Output Voltage vs. Time of Inverter x4 with Differing Loads and Square Wave Input



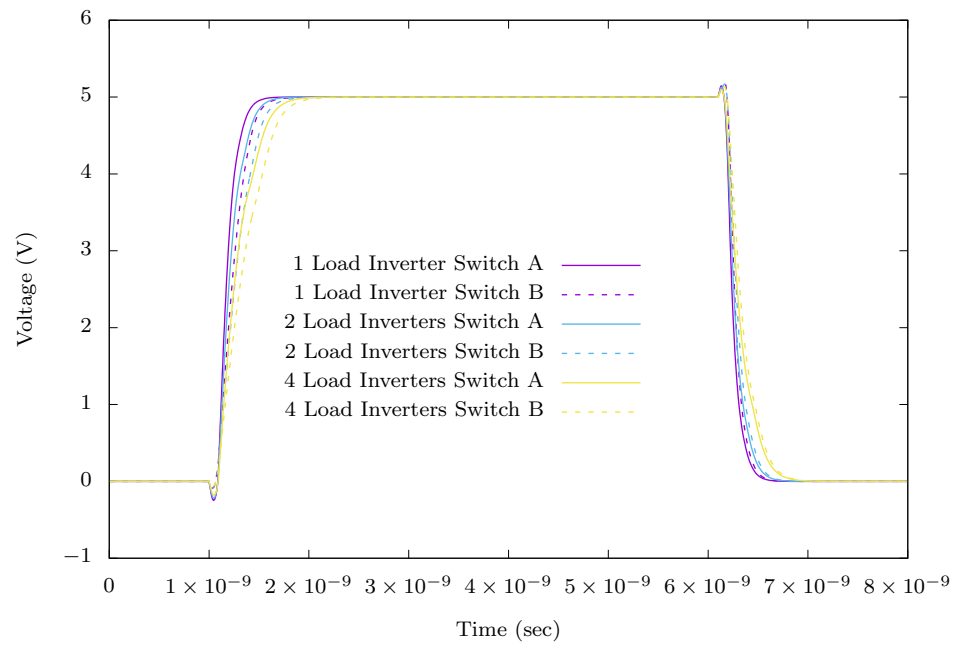Output Voltage vs. Time of Nand Gate with Differing Loads and Square Wave Input



Output Voltage vs. Time of Nor Gate with Differing Loads and Square Wave Input

